
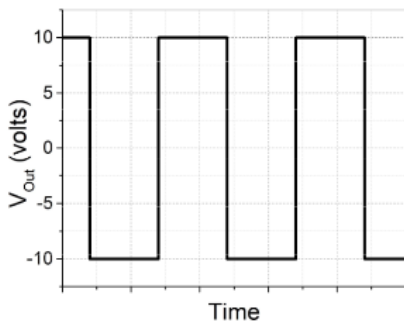
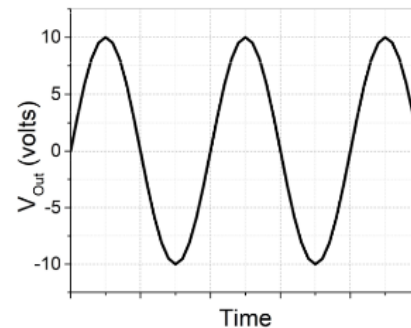
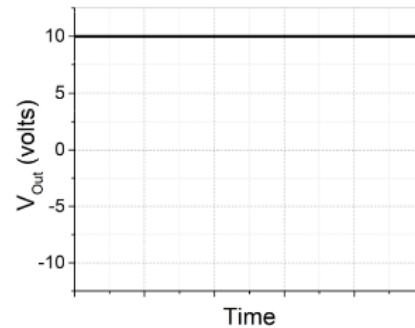


GATE 2022-PH

EE23BTECH1205 - Avani Chouhan*

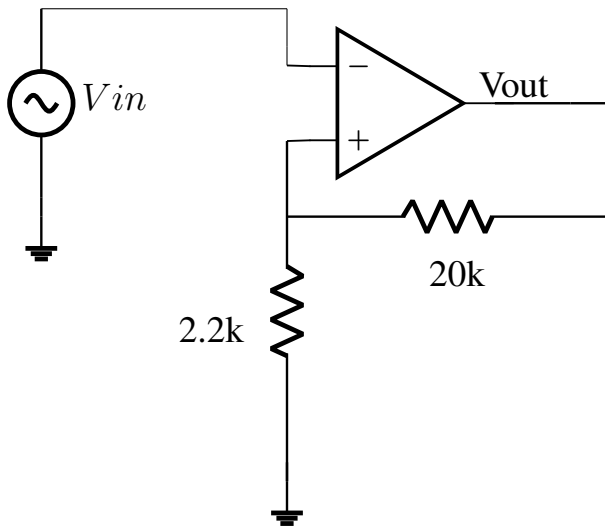Question : 11

For the Op-Amp circuit shown below, choose the correct output waveform corresponding to the input $V_{in} = 1.5 \sin(20\pi t)$ (in Volts). The saturation voltage for this circuit is $V_{sat} = \pm 10$ V.



- (A)
- (B)
- (C)
- (D)

(GATE PH 2022)

Solution:

Given circuit is a Schmitt Trigger circuit. In this output will be always saturated, i.e., limited between

$+V_{sat}$ to $-V_{sat}$.

Let's assume initially the output is at its negative saturation voltage ($-V_{sat}$). As the input voltage (V_{in}) increases, it eventually exceeds V_{TH} , causing the output of the op-amp to switch to its positive saturation voltage ($+V_{sat}$). As V_{in} decreases, it eventually falls below V_{TL} , causing the output of the op-amp to switch back to its negative saturation voltage ($-V_{sat}$). This process repeats as the input voltage oscillates sinusoidally. Each time V_{in} crosses one of the threshold levels, the output switches between $+V_{sat}$ and $-V_{sat}$.

So, the correct answer is (A).

